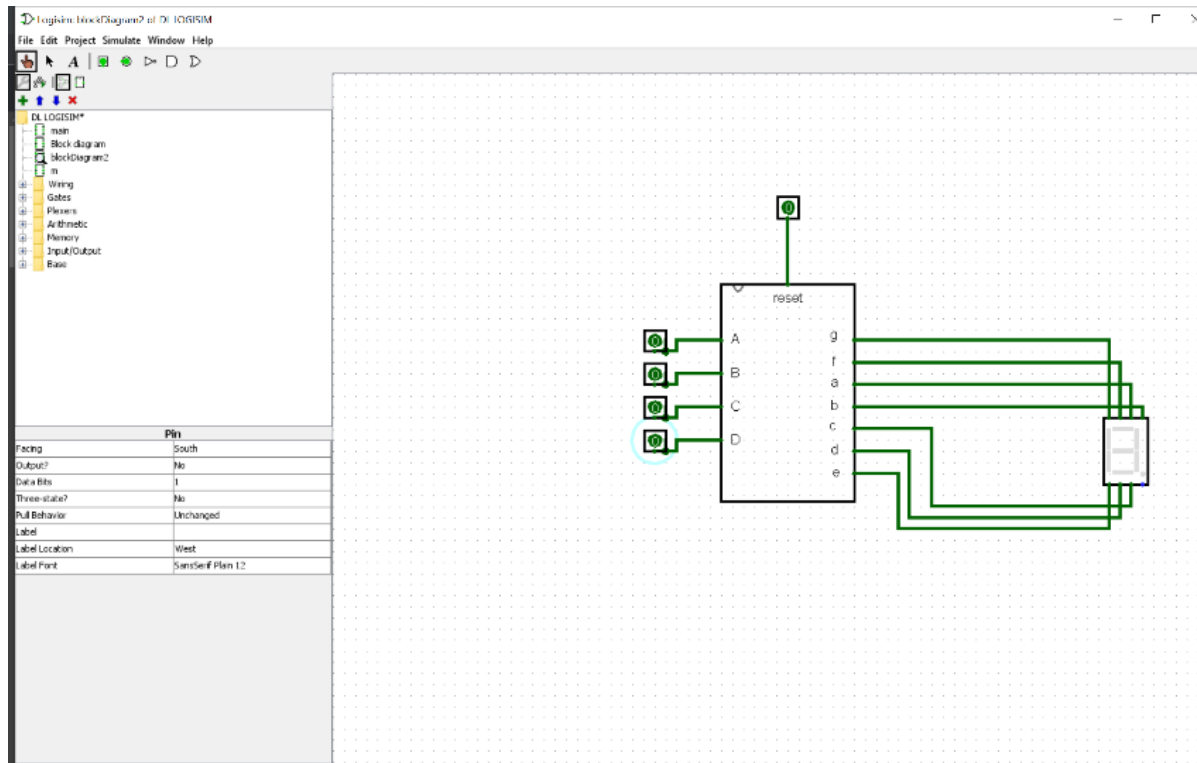


**-We designed and simulated a 7 segment display circuits:**

- The block diagram containing 4 inputs and 7 outputs (explained in the next page)



The 7-segment display was used in old calculators and computers to display the numbers from 0 to 9, in order to count 10 numbers in binary we're going to need 4 inputs that we represented by (A, B, C, D)

And 7 outputs (a, b, c, d, e, f, g), each '1' in the truth table represents the segment that will be enabled


**-First**, we needed to draw a truth table

$$2^4 = 16$$


NOTE: (The decimal digits from 10 to 15 are don't care because we can't display them in the 7-segment display)

Decimal Digit	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1

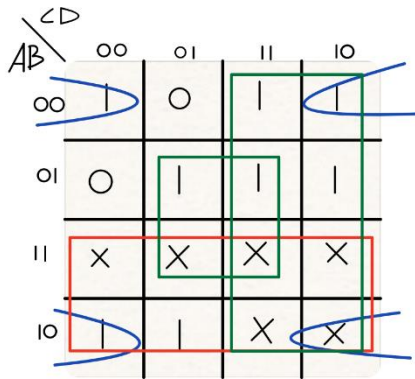
- **Second**, for each output we drew a  $2^4$  k-map and extracted an equation from each one by taking the biggest groups possible for better simplification:




$$a = A + C + BD + \overline{BD}$$

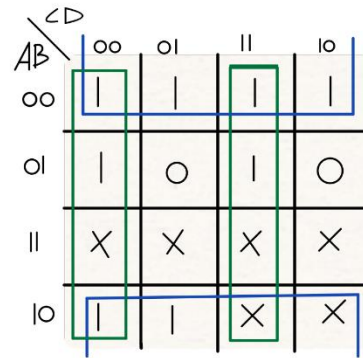

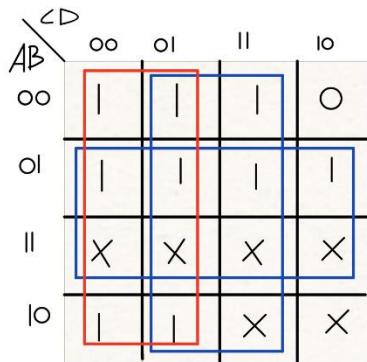
$$b = \overline{B} + \overline{C}\overline{D} + CD$$




$$c = B + \overline{C} + D$$

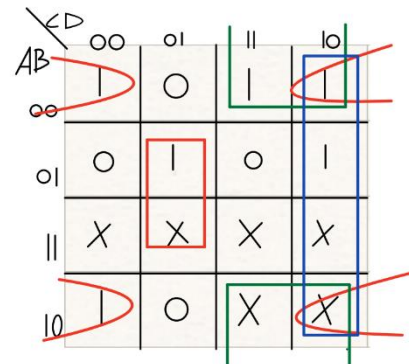

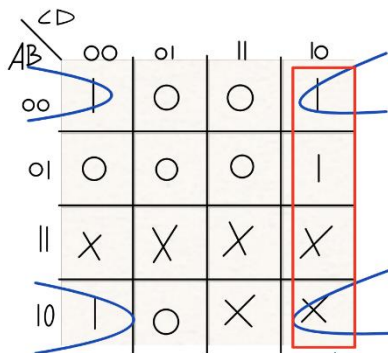
$$d = \overline{BD} + \overline{C}\overline{D} + \overline{B}\overline{C}D + \overline{B}C$$


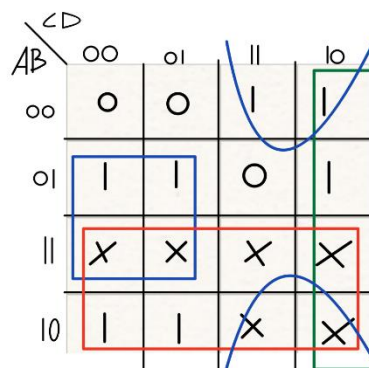
$$e = \overline{BD} + \overline{C}\overline{D}$$



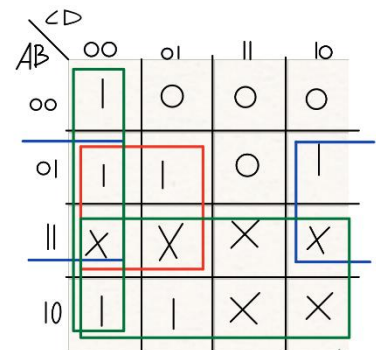
$$g = \overline{BC} + \overline{C}\overline{D} + \overline{B}\overline{C} + A$$




$$f = A + \overline{C}\overline{D} + \overline{B}\overline{C} + \overline{BD}$$

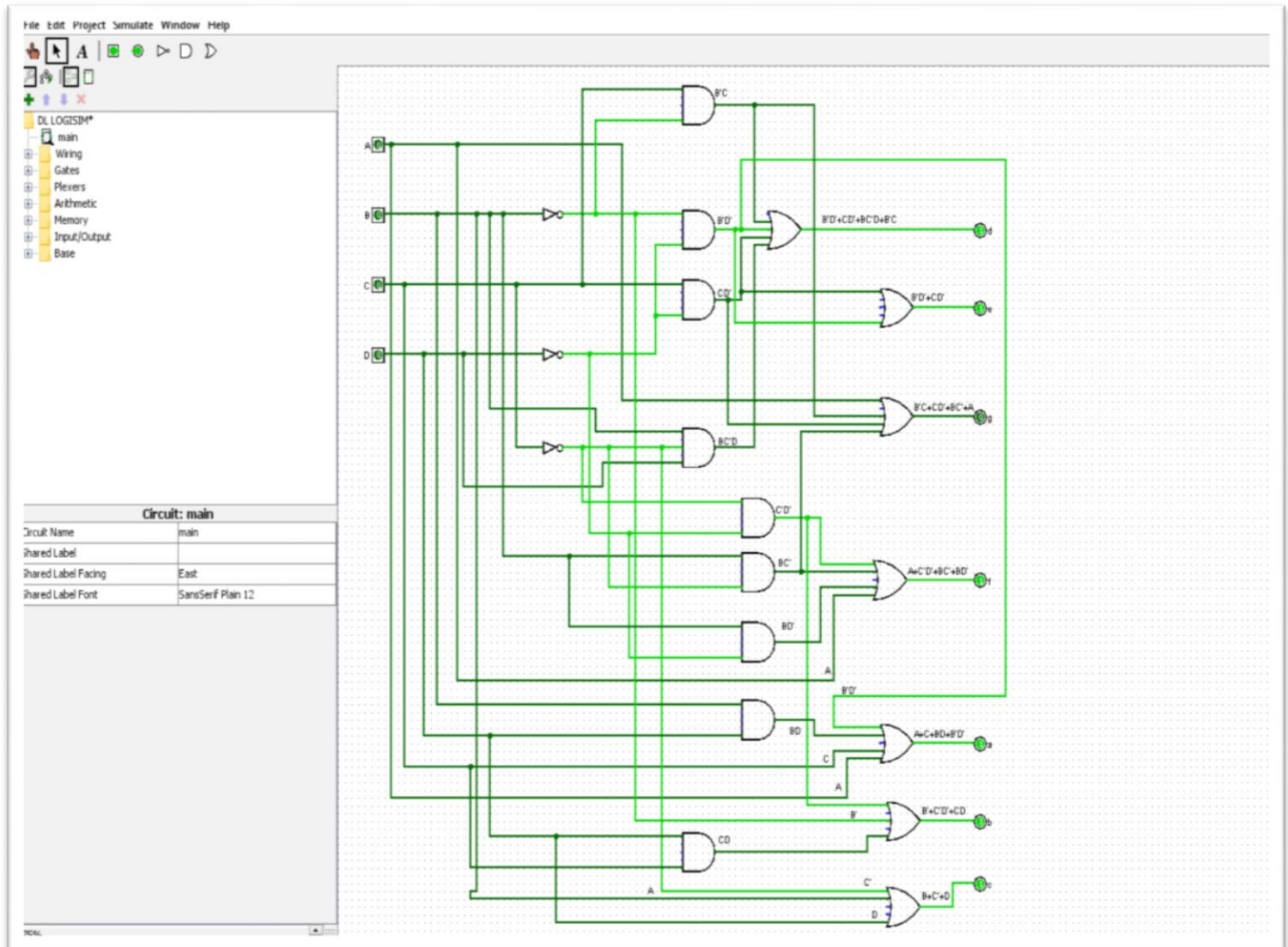-**Third**, we simulated each equation from the outputs and generated a circuit by using Logisim:




-Lastly, we dragged a 7-segment display to output each number from 0 to 9 by enabling or disabling the inputs and using a Reset:

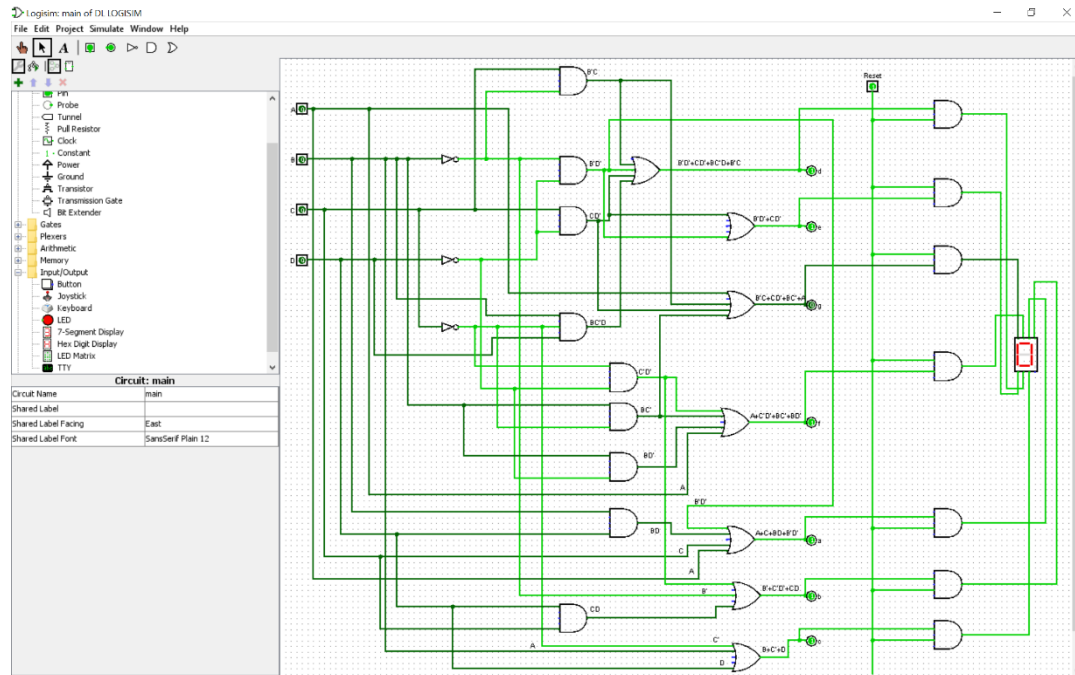
- when disabling all the segments we get 0



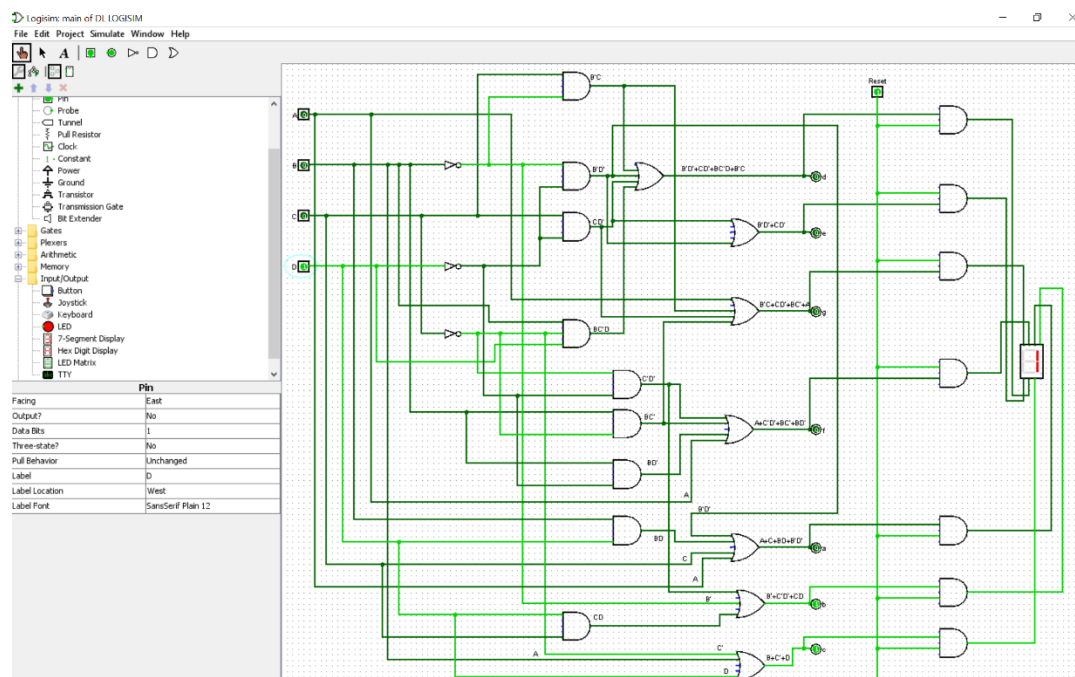
- Enabling just 'D' and disabling the rest we get 1



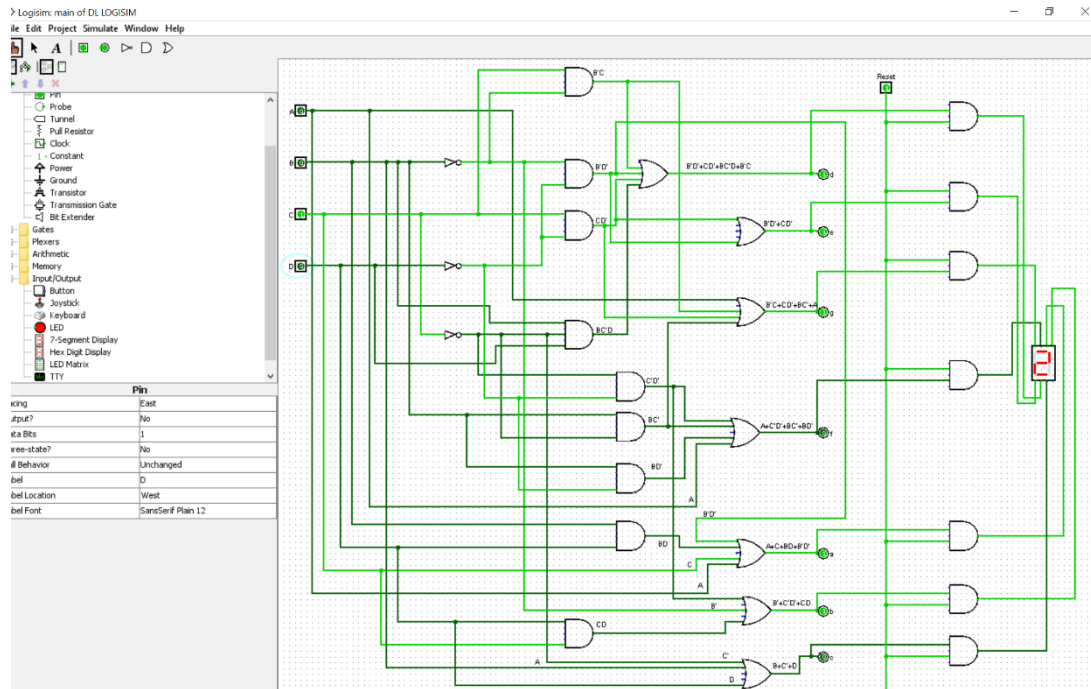- Enabling just 'C' and disabling the rest will give us 2




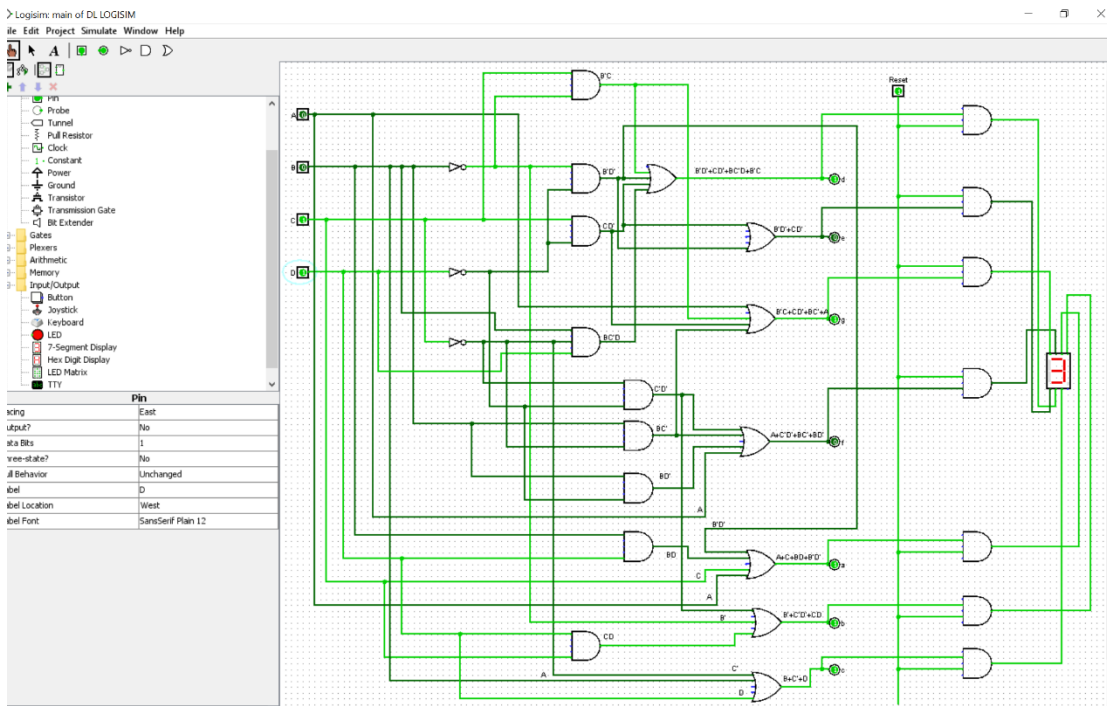- Enabling 'D' & 'C' and disabling the rest will give us 3






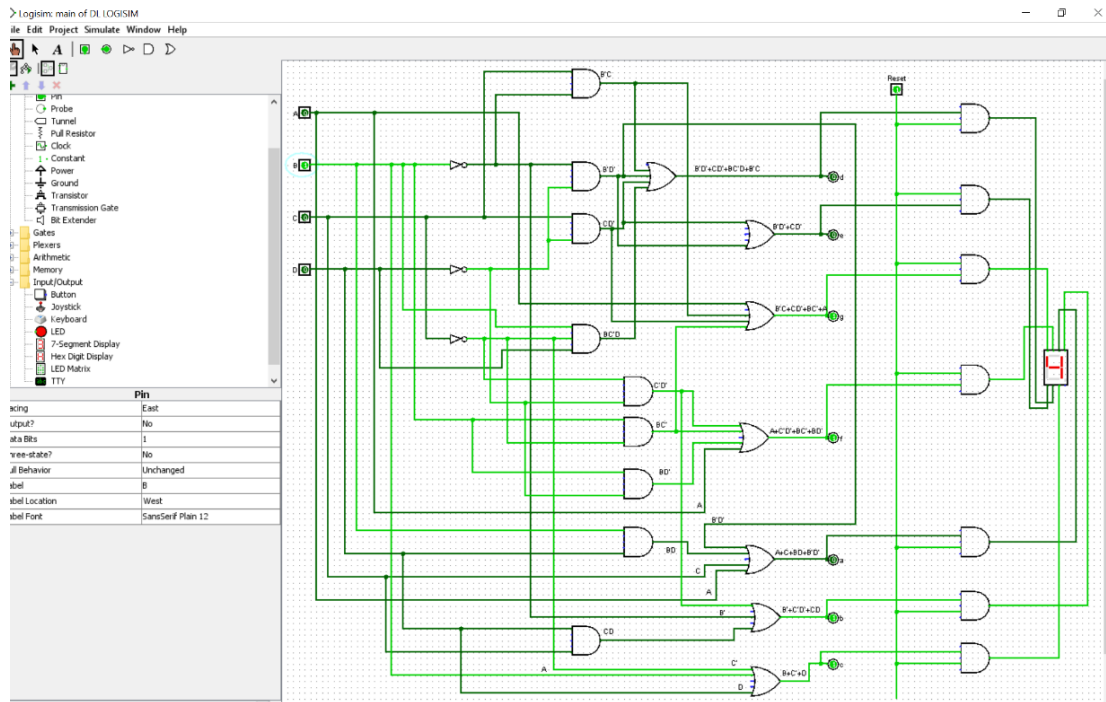
- Enabling just 'B' and disabling the rest will give us 4



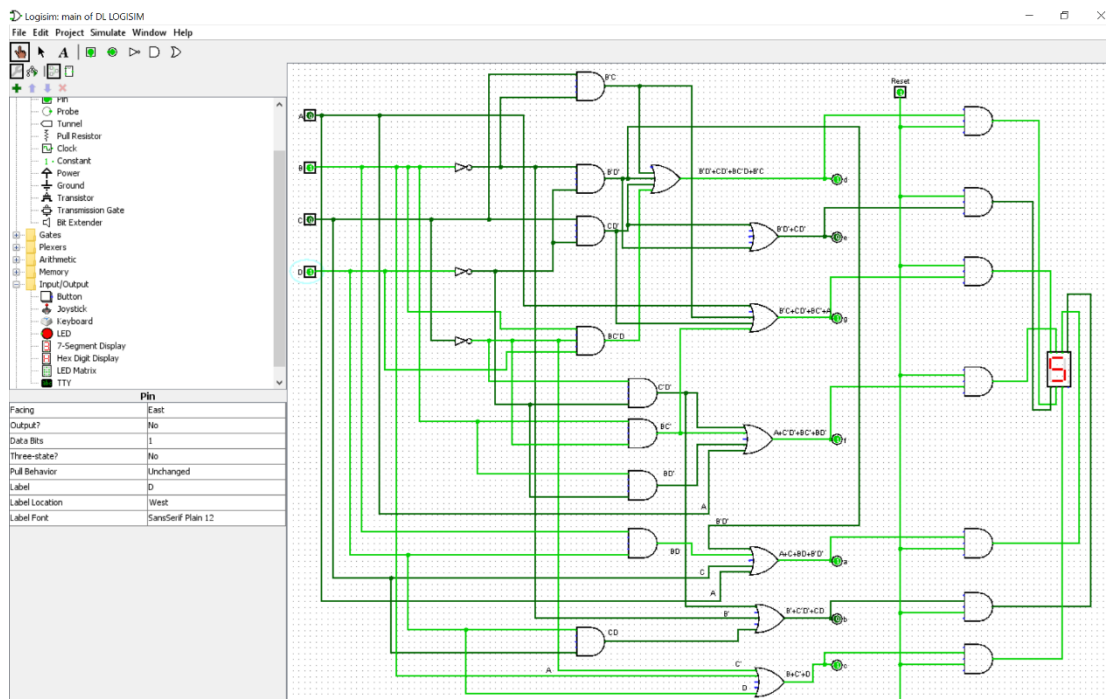
- Enabling 'B' & 'D' and disabling the rest will give us 5



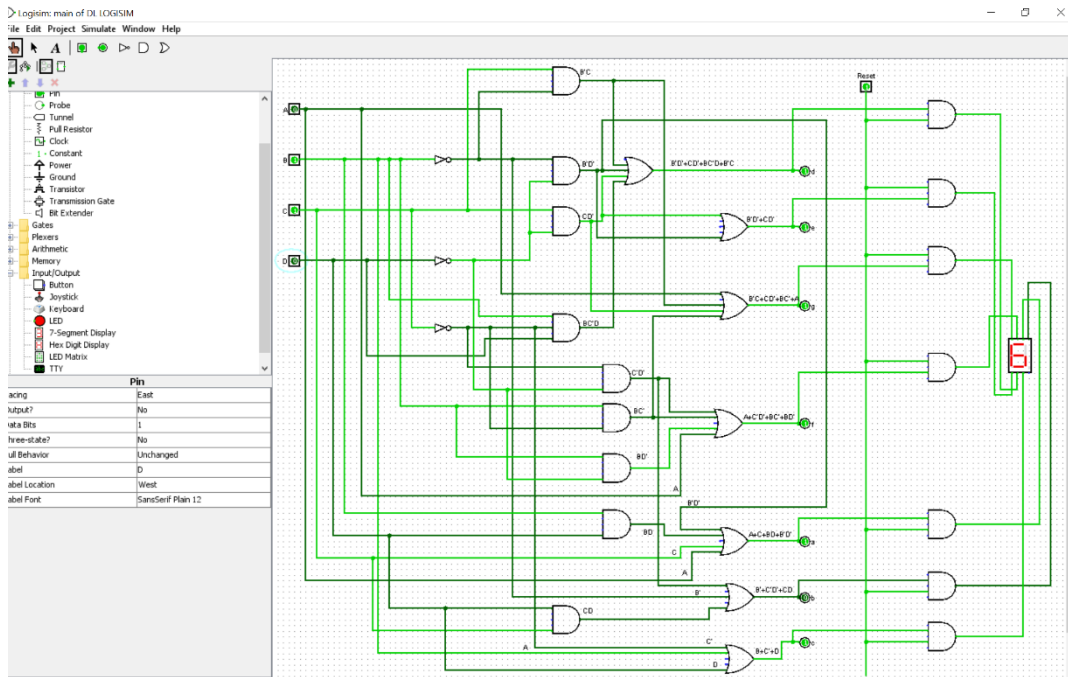- Enabling 'B' & 'D' and disabling the rest will give us 6




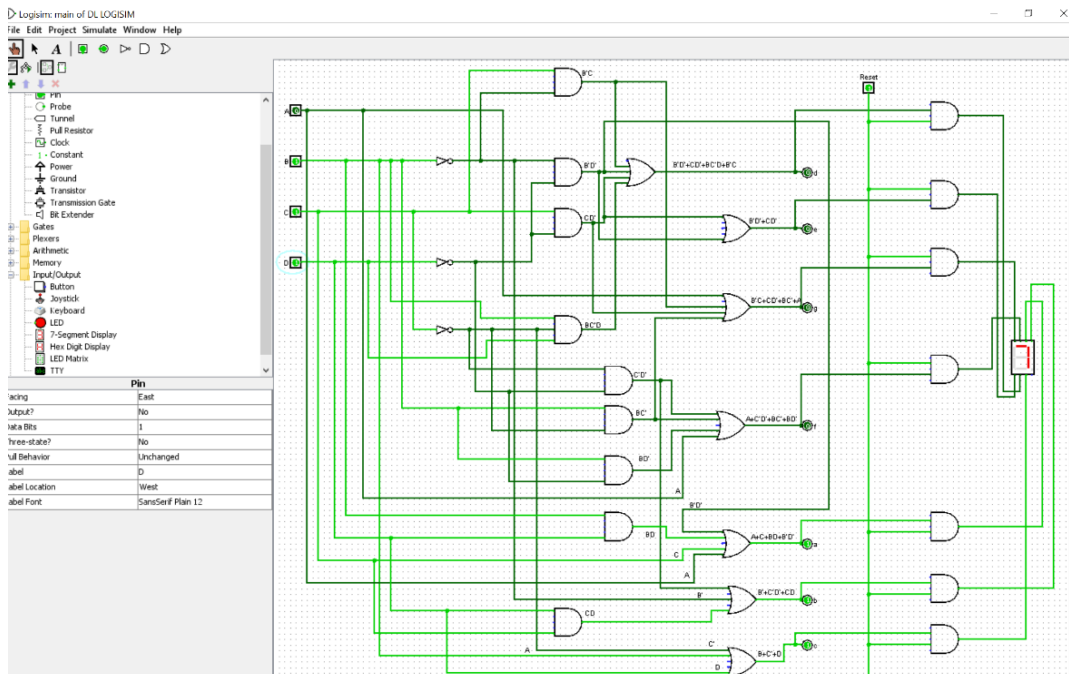- Enabling 'B' & 'C' & 'D' and disabling just 'A' will give us 7






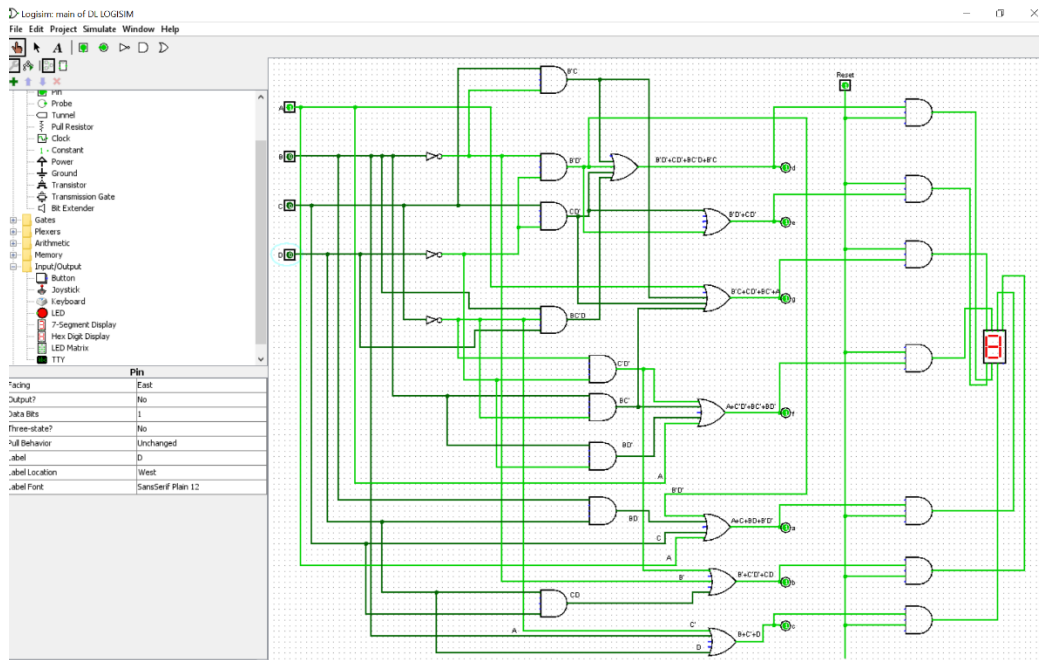
- Enabling just 'A' and disabling the rest will give us 8



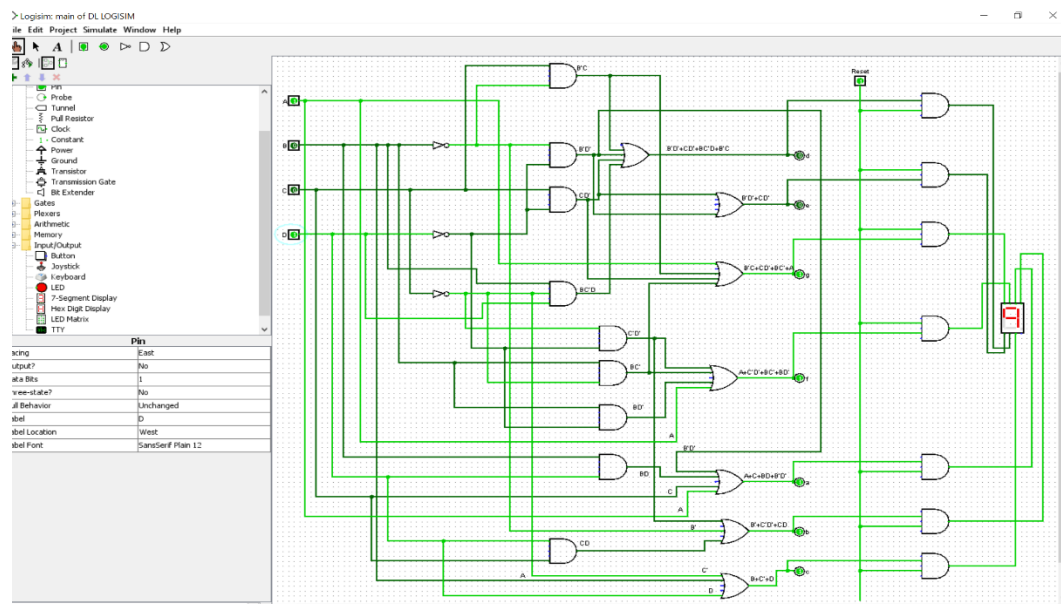- Enabling 'A' & 'D' and disabling the rest will give us 9



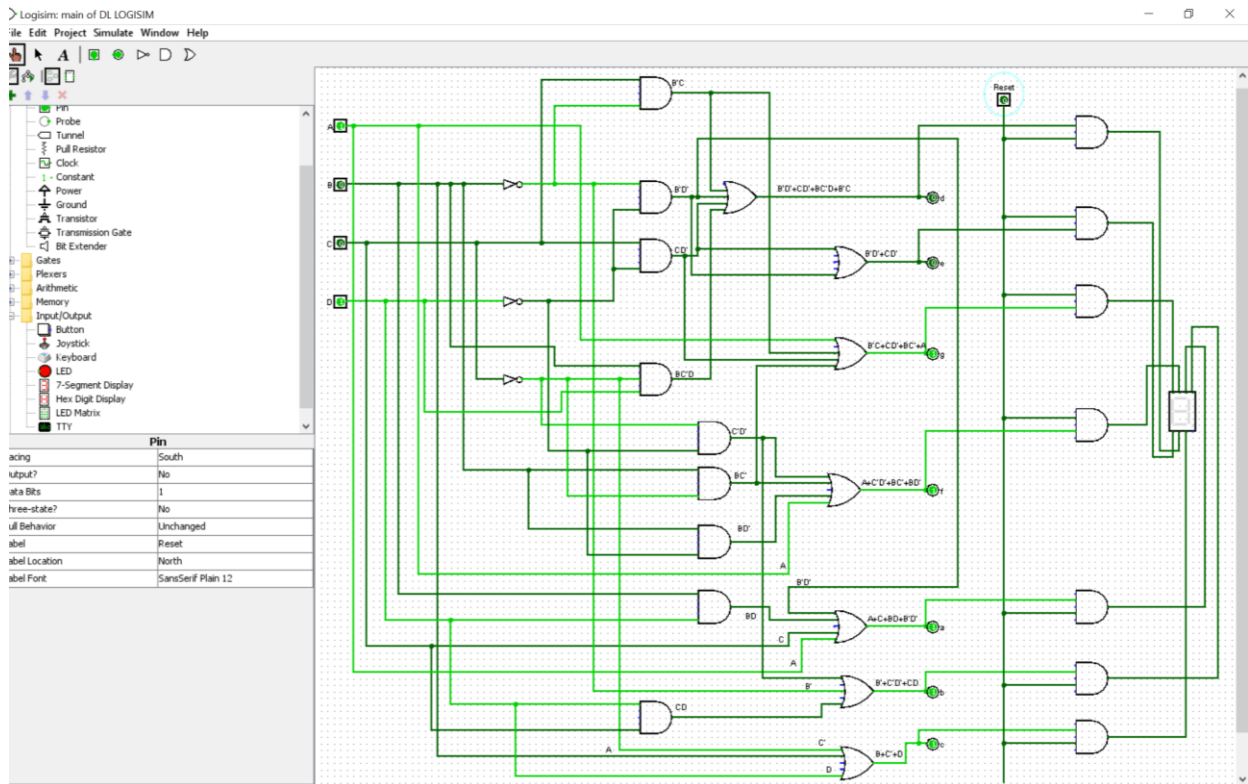- when disabling the 'Reset' the entire circuit will stop working



- The block diagram with the 7-segment display on

